

# Digital Design Diploma

## Assignment 1

### Combinational Circuit Design

<b>Name</b>	كریم حسن عاطف علي
<b>Group</b>	G2

**Submitted to: Eng. Kareem Waseem**

1)

```
Q1.v > Q1
1  module Q1 (input A,B,C,D,E,F,sel, output out,out_bar);
2  wire w0,w1;
3  assign w0= A&B&C;
4  assign w1= ~(D^E^F);
5  assign out = (sel) ? w1 : w0;
6  assign out_bar = ~out;
7  endmodule
```

Figure 1: Q1 Code

 


Figure2: Q1 Wave

2)

```
Q2.v > Q2
1  module Q2 (input A,B,C,sel, input [2:0] D, output reg out,out_bar);
2  reg w0,w1;
3  always @(*) begin
4  w0= (D[0] & D[1]) | D[2];
5  w1= ~(A^B^C);
6  out = (sel) ? w1 : w0;
7  out_bar = ~out;
8  end
9  endmodule
```

Figure 3: Q2 Code

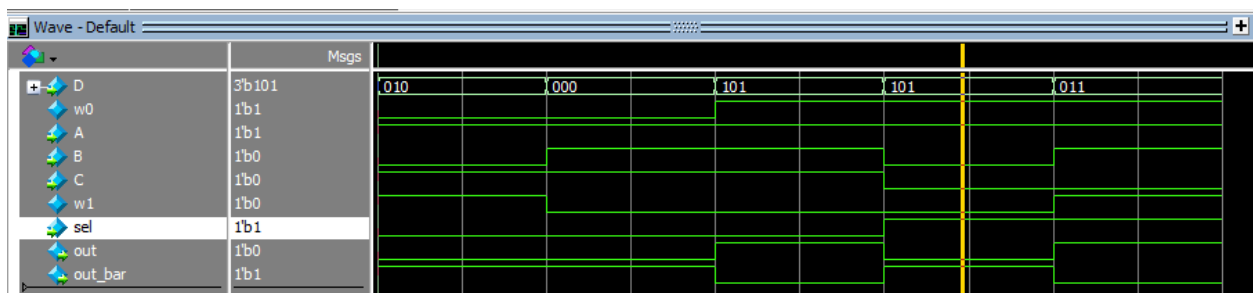


Figure 4: Q2 Wave

3)

```

Adder 4-bits.v > Adder_4bits
1  module Adder_4bits (input [3:0] A,B, output [3:0] C);
2  assign C = A + B;
3  endmodule

```

Figure 5: Q3 Code

	Msgs						
A	4'b1010	1010	1101	1001	0110		
B	4'b0001	0001	0000	1111	1100		
C	4'b1011	1011	1101	1000	0010		

Figure 6: Q3 Wave

4)

```

Decoder 2x4.v
1  module Decoder2x4 (input [1:0] A, output [3:0] D);
2  assign D = (A==2'b00)? 4'b0001 :
3             (A==2'b01)? 4'b0010 :
4             (A==2'b10)? 4'b0100 :
5             (A==2'b11)? 4'b1000 : 4'b0000;
6  endmodule

```

Figure 7: Q4 Code

	Msgs					
A	2'd1	0	1	2	3	1
D	4'b0010	0001	0010	0100	1000	0010

Figure 8: Q4 Wave

5)

```

Even Parity.v > Even_Parity
1  module Even_Parity (input [7:0] A, output [8:0] out_with_parity);
2  assign out_with_parity = {A, ^A};
3  endmodule

```

Figure 9: Q5 Code

A	8'b00011100	01010010	10010010	10010011	00011100	
out_with_parity	9'b000111001	010100101	100100101	100100110	000111001	

Figure 10: Q5 Wave

6)

```

1  module ALU_with_7Segment_display #(parameter WIDTH = 4)
2  (input [WIDTH-1:0] A, B, input [1:0] opcode, input Enable, output reg a,b,c,d,e,f,g);
3
4  wire [WIDTH-1:0] result;
5
6  //N_bit_ALU #(parameter N=4) (input [N-1:0] in0,in1, input [1:0] opcode, output reg[N-1:0] out);
7  N_bit_ALU #(.N(WIDTH)) ALU(.in0(A), .in1(B), .opcode(opcode), .out(result));
8
9  always @(*) begin
10     if (Enable) begin
11         case (result)
12             4'b0000: {a,b,c,d,e,f,g} = 7'b1111110; // 0
13             4'b0001: {a,b,c,d,e,f,g} = 7'b0110000; // 1
14             4'b0010: {a,b,c,d,e,f,g} = 7'b1101101; // 2
15             4'b0011: {a,b,c,d,e,f,g} = 7'b1111001; // 3
16             4'b0100: {a,b,c,d,e,f,g} = 7'b0110011; // 4
17             4'b0101: {a,b,c,d,e,f,g} = 7'b1011011; // 5
18             4'b0110: {a,b,c,d,e,f,g} = 7'b1011111; // 6
19             4'b0111: {a,b,c,d,e,f,g} = 7'b1110000; // 7
20             4'b1000: {a,b,c,d,e,f,g} = 7'b1111111; // 8
21             4'b1001: {a,b,c,d,e,f,g} = 7'b1111011; // 9
22             4'b1010: {a,b,c,d,e,f,g} = 7'b1110111; // A
23             4'b1011: {a,b,c,d,e,f,g} = 7'b0011111; // B
24             4'b1100: {a,b,c,d,e,f,g} = 7'b1001110; // C
25             4'b1101: {a,b,c,d,e,f,g} = 7'b0111101; // D
26             4'b1110: {a,b,c,d,e,f,g} = 7'b1001111; // E
27             4'b1111: {a,b,c,d,e,f,g} = 7'b1000111; // F
28             default: {a,b,c,d,e,f,g} = 7'b0000000; // Off for other values
29         endcase
30     end
31     else begin
32         {a,b,c,d,e,f,g} = 7'b0000000; // Off when Enable is low
33     end
34 end
35 endmodule

```

Figure 11: Q6 Code

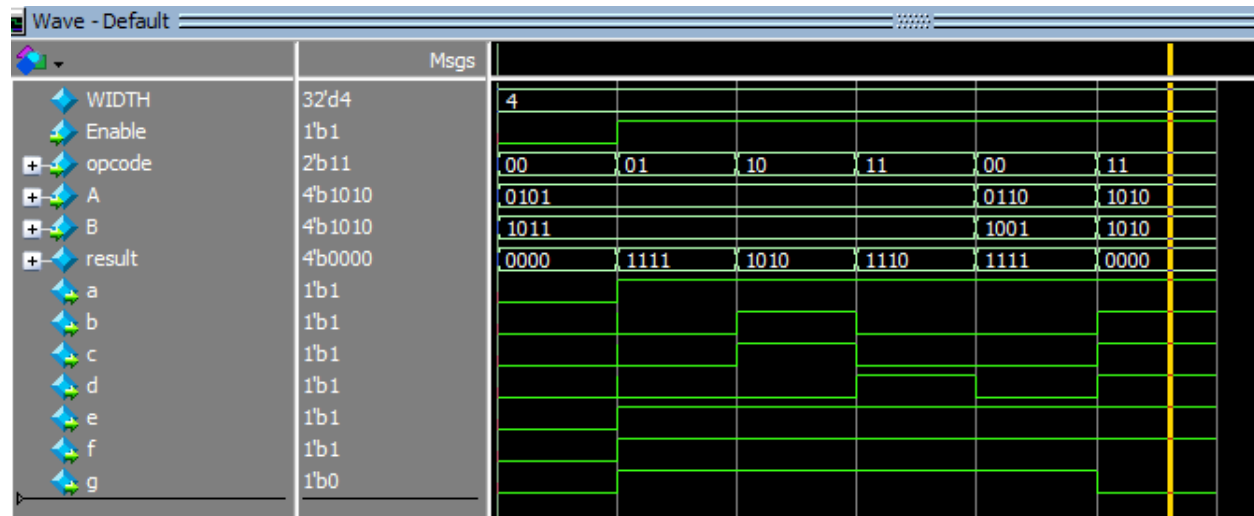


Figure 12: Q6 Wave